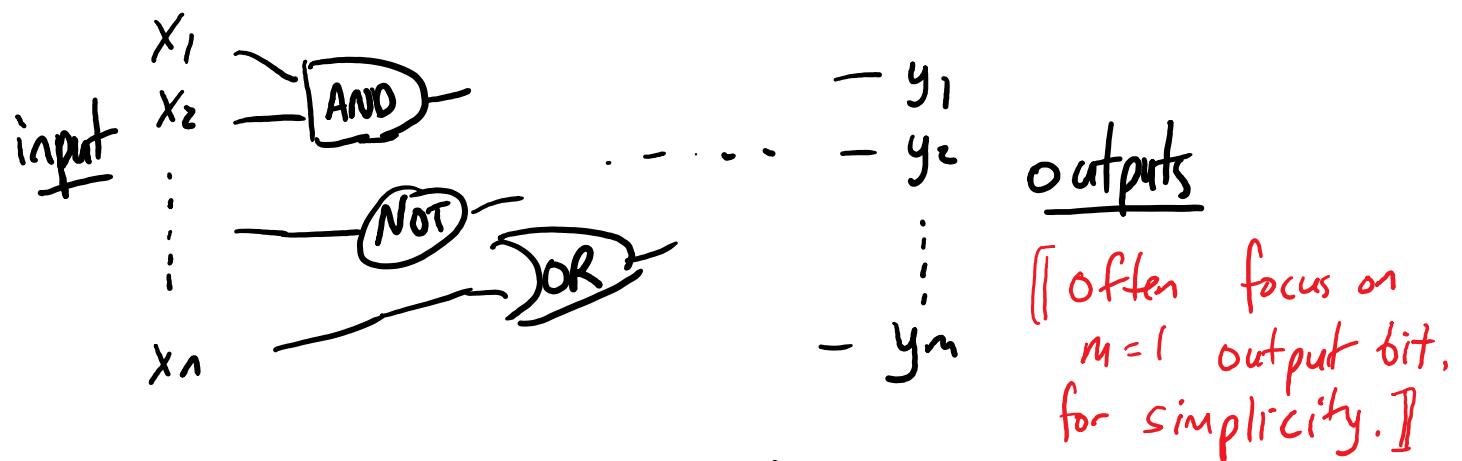


# Lecture 10: Basics of Quantum Computing

[In fact, let's start with basics of classical computing]

[Quantum computing is most clearly & naturally done in the "circuit model" we've been using, so let's do our classical computing in this model too to have clear comparison.]

Classical Circuit C:



Computes a fcn.  $F: \{0,1\}^n \rightarrow \{0,1\}^m$

[E.g.: take an n-bit #, want to output 0/1 ( $m=1$ ) depending on if it's prime or not.]

Focus on efficiency: # of gates,  
and how it  
scales with n

[Could consider other measures too, but let's keep it simple.]

Gates  $\approx$  steps/time.


[Certainly steps/time  $\leq$  Gates.

Possible that time  $\ll$  gates if you can parallelize effectively. Important in practice, but let's ignore for now.]

[You might be more used to doing your classical computing in, say...]

python:
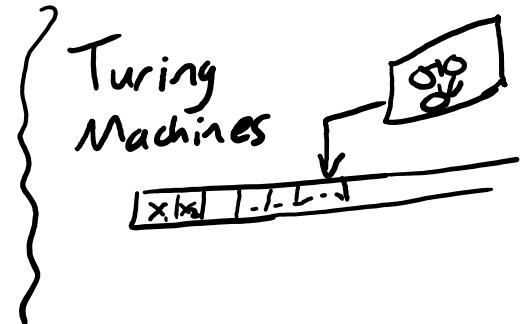
```
def C(x):  
    ...  
    return y
```



fact/thm: Given python code computing  $F$  on length- $n$  inputs in  $T$  "time steps", can (easily) produce circuit computing  $F$  with  $\leq \text{const}_{\text{Python}} \cdot T \cdot \log T$  gates

[Main term  $\overline{T} \cdot \log T \leq 100$  in life,  $\text{const}_{\text{Python}} \leq 100$ ? Diff. constant for TMs, Java, etc., but indep. of  $T, n$ , etc.]

## (Claude) Shannon's Theorems, '37 (master's thesis)

- Every  $F: \{0,1\}^n \rightarrow \{0,1\}$  can be computed by an AND/OR/NOT circuit with  $\leq 2^n$  gates ( $\approx 2^n/n$  in fact)  
*[Not great. Unphysically large for  $n >$  few hundred]*
- Almost all such  $F$  need  $\geq \frac{2^n}{n}$  gates  
*[So almost all funcs are effectively uncomputable in real life.  
Fortunately, we care about computing specific, interesting functions. And sometimes (not always) they can be computed efficiently/physically/in P:  
 $\propto n$  or  $n^2$  or  $n^3$  gates...]*

## Aside: Probabilistic Computing (cf. Lecture 2)

- Adds a  gate

[No inputs, 1 output.]

- output  $\begin{cases} 0 & \text{with prob. } \frac{1}{2} \\ 1 & \text{with prob. } \frac{1}{2} \end{cases}$

Prob'ic circuit  $C$  "computes"  $F$  if


for all  $x \in \{0, 1\}^n$ ,

$\Pr_{\text{flips}} [C(x) \neq F(x)]$  is "small";  
say  $\leq 1\%$

[You explored all this, & 0-sided, 1-sided,  
2-sided error, in HW #1, Problem #5.]

[Recall from Loc. 2: believed to not help  
much for efficiency. Not believed that  
there are  $F$  computable in  $P$  with  
randomness but not in  $P$  deterministically.]

[finally!] Quantum Computing

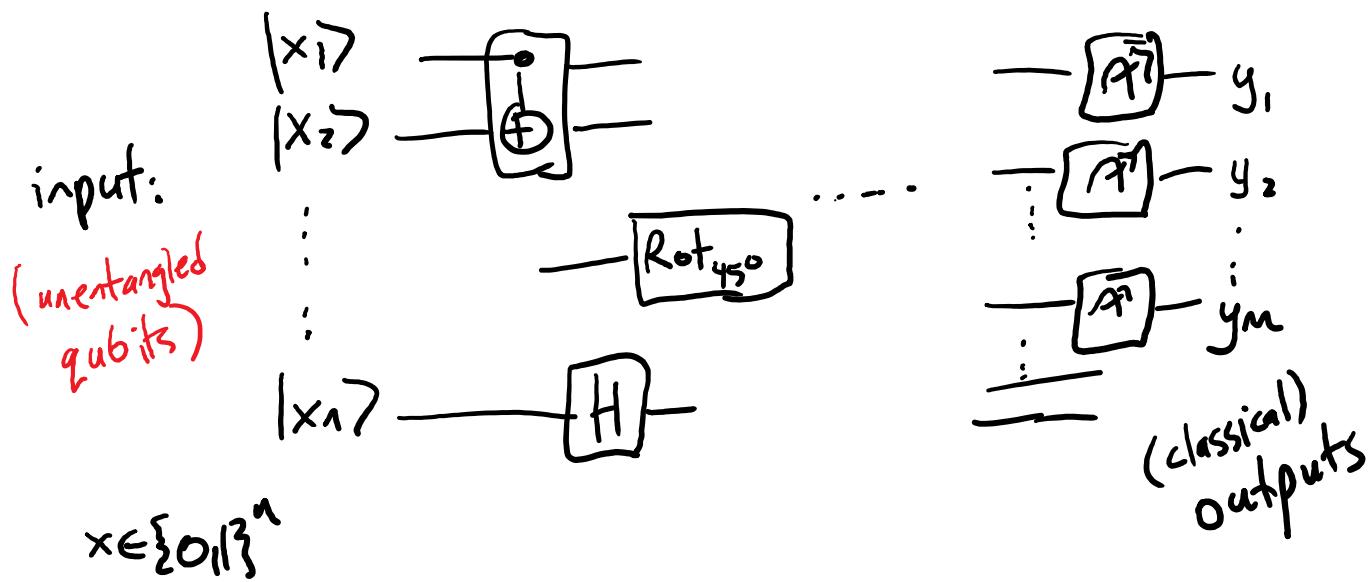

Computes  $F: \{0,1\}^n \rightarrow \{0,1\}^n$  if...

<same as in probabilistic computing>

[Rem: WLOG all measurements at end, by "Principle of Deferred Measurement": HW5, #2.]

Q1: ? F which quantum computers can compute much more efficiently than classical comps?

[A1: seemingly yes, e.g. Factoring. Half-dozen lectures from now.]

Q2: Reverse question! [A2: No. Today we'll see that Q.C.'s are at least as powerful as classical comps.]

Q3: Does the exact quantum gate set matter?

[A3: Not really, but a little subtler than classical case. Next lecture---]

# Q.C.s ≥ Classical Comps?

Can a QC. even compute  $x_1 \text{ AND } x_2$ ?

[In fact, not directly, no! Recall...]

Q. gates are unitary:  $UU^\dagger = I$   
 $\Rightarrow U^\dagger = U^{-1}$

$U$  is invertible / reversible

(In fact, almost all q. gates we've seen -  
NOT, Z, H, CNOT, ... are their own inverse.  
Roto gates an exception.)

AND: not reversible:  $00, 01, 10 \rightarrow 1.$

"erases information"  $\xleftarrow{?}$

[Same with OR. On the other hand...]


NOT: is reversible [In fact, it is a quantum gate.]

Reversible computation was a topic studied by physicists in '60s, '70s, ... independent of quantum. Key early figure: Ralf Landauer @IBM. Physicists tried to understand the theoretical min. energy needed to do a "step" of computation. Landauer saw that it wasn't computation that req'd energy per se — it was "erasing info." Classical laws of physics are time-reversible. In principle, a reversible computation — like a NOT (or a CNOT) can be done in a "closed system" w/ no energy loss. A non-reversible op., like AND, "erases info" → "loses entropy" → by 2nd law of thermodynamics it must go somewhere → can't be a "closed system" → must leak, say, heat. Physicists thought: if you can make computation fully reducible, in principle it requires no min. energy. In practice, '70s & '80s saw very energy-efficient non-reversible computers, so idea ended up unnecessary. Apparently it's making a comeback these days, though.]

[Key names in reversible computing: Yves Lecerf (French-Syrian ethnologist!!), Fredkin, Toffoli, Feynman, Bennett, Huffman, Lovens...]
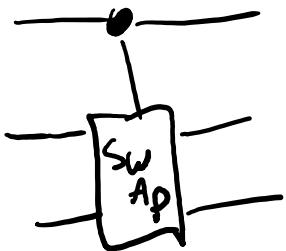
# Useful reversible gate: CSWAP

[[Controlled-SWAP; aka "Fredkin gate"; HW#3, #1]]




[[As usual: if control bit is 0, do nothing, pass all bits thru. If control bit is 1, pass it thru & swap other two bits.]]

$$|000\rangle \rightarrow |000\rangle, \dots |110\rangle \rightarrow |011\rangle, |111\rangle \rightarrow |111\rangle$$


[[Easy to see it's reversible. In fact, easy to see it's...]] self-inverse.

8x8 permutation mtx, hence unitary matrix.  
(So, like NOT, CNOT, and SWAP, can think of it as a reversible classical gate, and also as a 3-qubit quantum gate. We'll assume we can physically build it.)

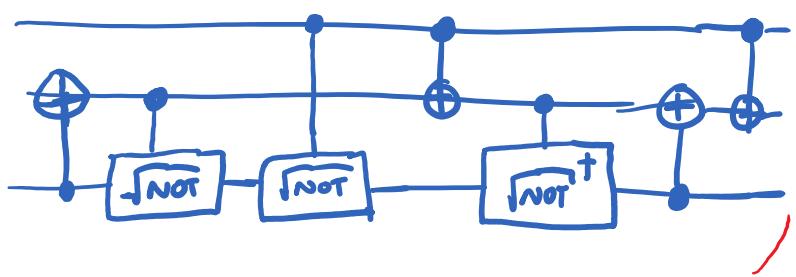
Here's one way,  
assuming you can  
build 2-qubit gates:



Now check this out: ]

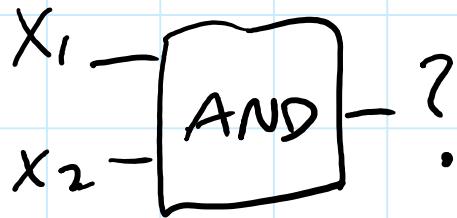

→

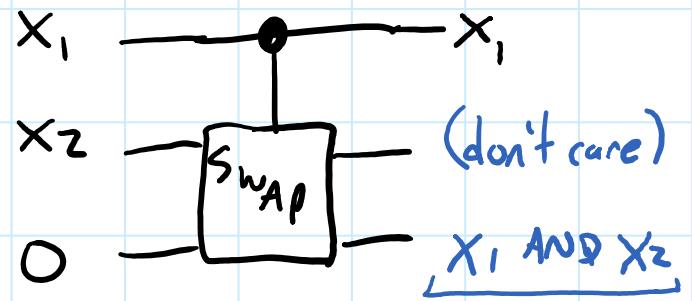


"ancilla"



[certainly, if  $x_1=0$ , it's O;  
if  $x_1=1$ , it's 1 iff  $x_2=1$ ]

[just a "catalyst" you plug in]

(don't care): "garbage"

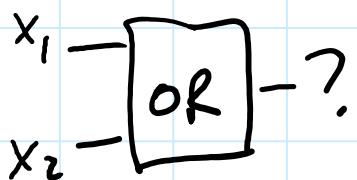


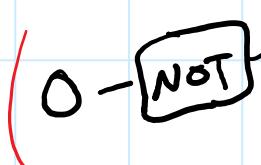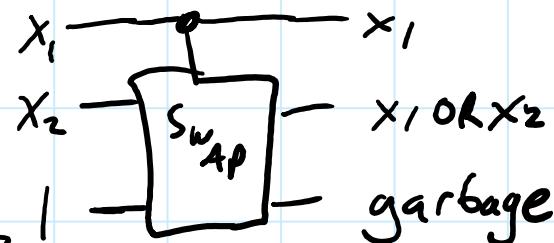[Well, by de Morgan's laws, can be  
built from AND & NOT, so  
who cares? But anyway, it's---]




[If you prefer all ancillas be 0,  
as is traditional.]

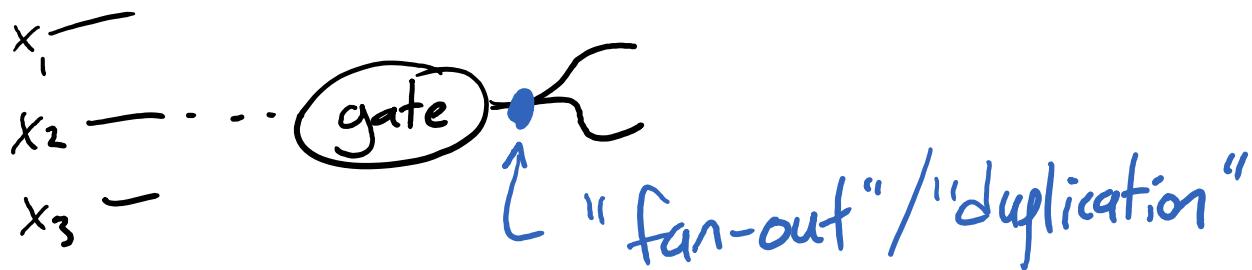(Are we done, for simulating classical circuits by quantum? No! One more "gate" that's rarely mentioned---)



(Traditionally you can just draw this in logic circuits, but it must actually correspond to a physical gadget.)

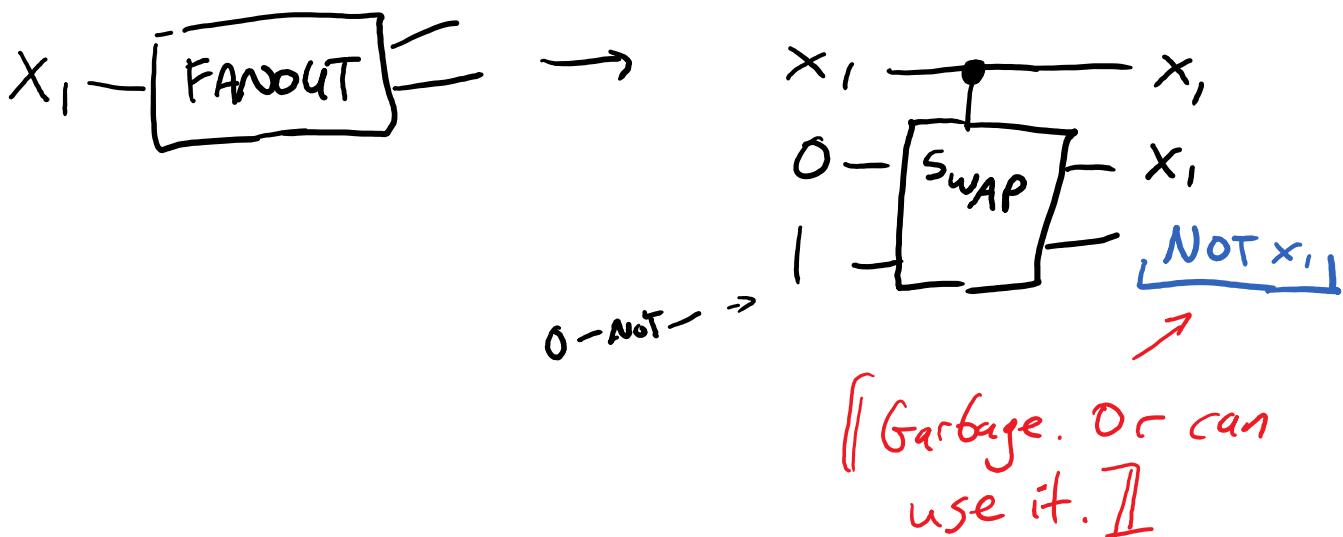(Luckily, can also sim. w/ CSWAP & ancillas.)



Fun: if you allow 0&1 ancillas, can use only CSWAPS to sim. AND, OR, NOT, FANOUT! ]

Thm: Any classical circuit  $C$  computing  $F: \{0,1\}^n \rightarrow \{0,1\}^m$  can be efficiently converted to a reversible (hence quantum) circuit

$$\text{QC}: \{0,1\}^{n+a} \rightarrow \{0,1\}^{m+g}, \quad n+a = m+g$$


$$(x, \underbrace{00\dots 0}_a) \mapsto (\underbrace{f(x)}_m, \underbrace{\text{garbage}(x)}_g)$$

(Can assume final output bits are in first  $m$  positions by doing SWAPS if nec.)

If orig. circuit had  $T$  gates, QC has  $O(T)$  gates & ancillas.

If inputs classical, final state has no superposition; measuring gives correct answer w/ 100% prob.)

Aside: FLIP?

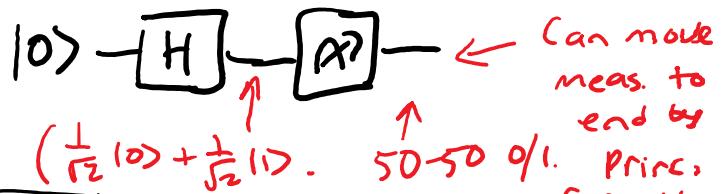

∴ Q.C.  $\supseteq$  classical (even probabilistic) computing

Puzzle:

$\exists$  efficient classical multiplication circuits,  
 $(P, Q) \longrightarrow P \cdot Q.$

Build the reversible version,  $C$ .

Then reverse it!

$$C^{\text{rev}}(P \cdot Q) = (P, Q)$$

$\rightarrow$  an efficient classical circuit for  
factoring?


(Answer ... no. Why not?)

Have to guess what garbage to  
put into  $C^{\text{rev}}$  to produce  
all-0 ancillas.

(In general, we don't like garbage. In fact,  
we'll later see that it's very bad to leave it  
around in q. computation. Can we get  
rid of it?)
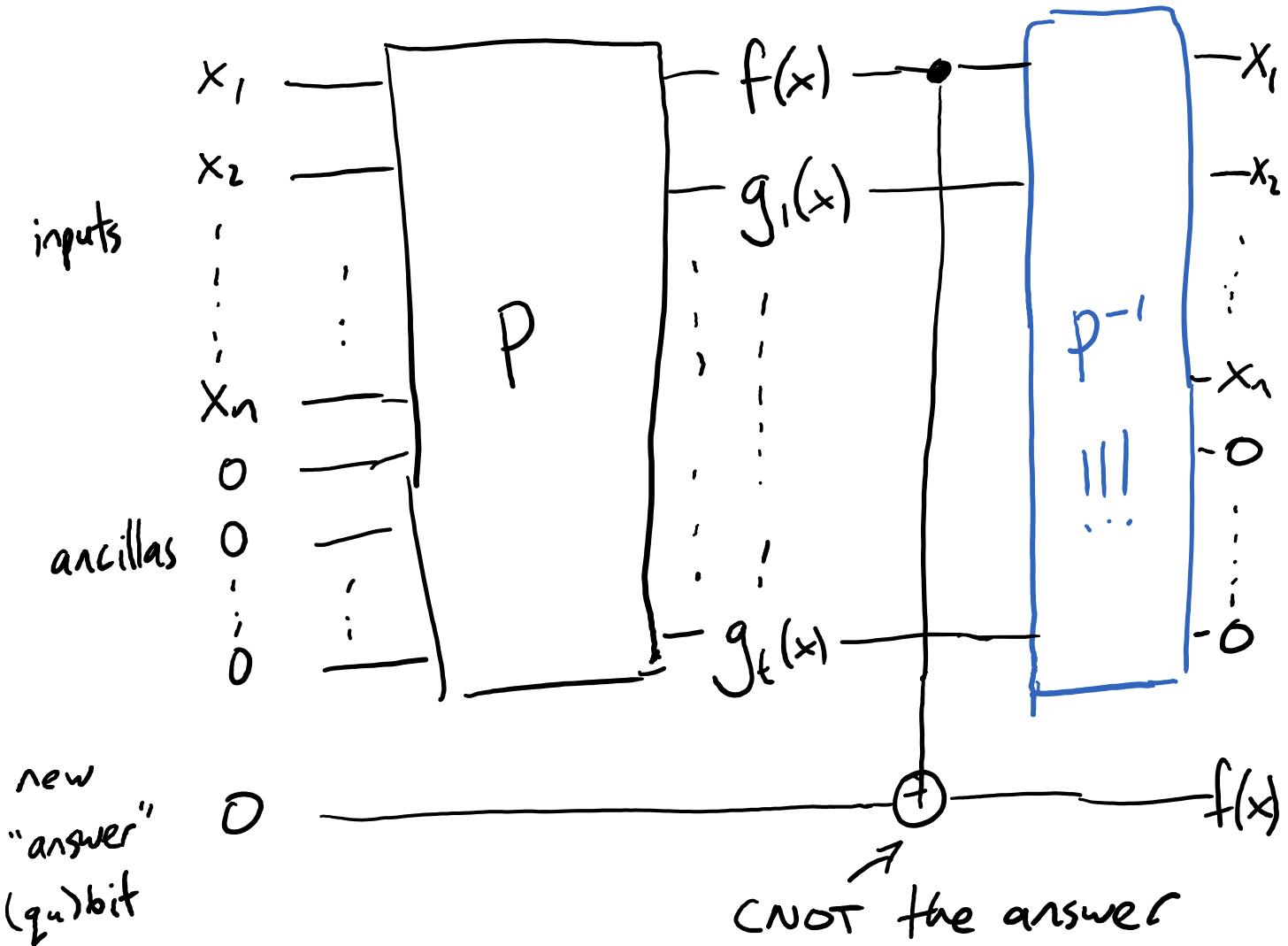
# Uncomputing Garbage [Bennett '80s]

Say  $F: \{0,1\}^n \rightarrow \{0,1\}$  [*1-bit output, for simplicity*]  
 computed reversibly/quantumly:



$$|x\rangle \otimes |0^a\rangle \otimes |0\rangle \rightarrow |x\rangle \otimes |0^a\rangle \otimes |f(x)\rangle$$

(Works for multi-bit outputs, too. Usually we add SWAPs to get answer first, ancillas last.)

Small remark: If answer bit(s) initialized to  $|y\rangle$  (instead of  $|0\rangle$ ), CNOT converts to...

$$|y \oplus f(x)\rangle$$

XOR (bitwise)

Overall:  $|x\rangle|y\rangle|0\dots\rangle \mapsto |x\rangle|y \oplus f(x)\rangle|0\dots\rangle$

(Puzzle: Now that garbage is uncomputed, can we reverse a multipl. circuit to get a factoring circuit? No: the orig. input is part of the final output.)

Def: A quantum circuit implements  $F: \{0,1\}^n \rightarrow \{0,1\}^m$  if it computes it in above garbage-free manner.

(So now we've seen that any classical circuit computing a fn  $F$  can easily be converted to a quantum circuit implementing  $F$ .)

(Remark: The ancillas are really now like a "catalyst". You have to put them in to get things to work, but in the end they just come out as unentangled  $|0\rangle$ 's. This is great for subroutine purposes. Can string Q. circuits together, no worry about ancillas/garbage interfering. Can actually reuse ancillas.

Eventually, we might lazily not even mention them, writing


$$|x\rangle|y\rangle \mapsto |x\rangle|y\oplus f(x)\rangle,$$

But truth is, there's always ancilla  $|0\rangle$ 's attached on both sides.)

(Quick preview of the power(?)  
of quantum computing.)

Say  $\boxed{QC}$  implements  $F: \{0,1\}^n \rightarrow \{0,1\}$ .

Build

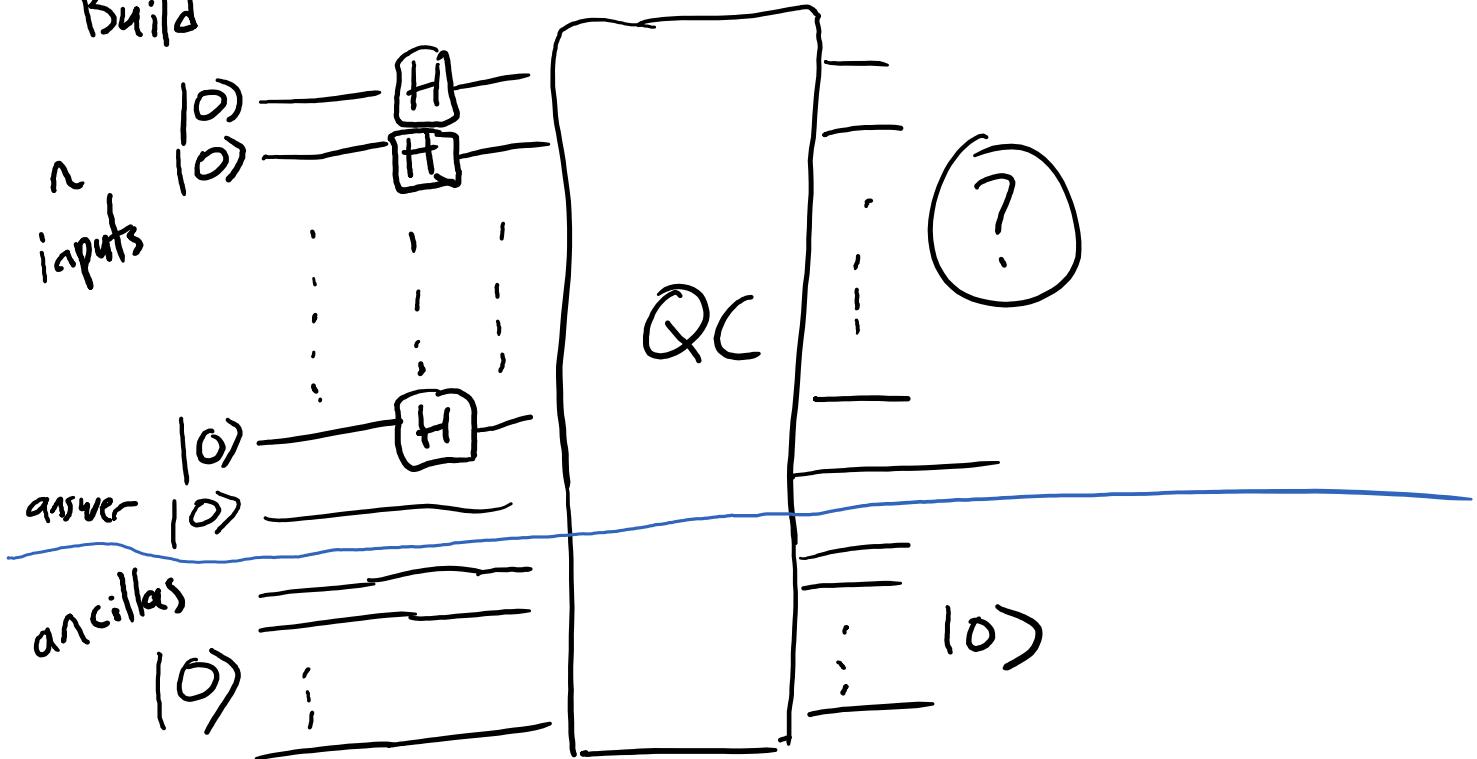

$$\begin{aligned} \text{Input state: } & (|+\rangle \otimes \dots \otimes |+\rangle) \otimes |0\rangle \\ &= \left(\frac{1}{\sqrt{2}}|0\rangle + \frac{1}{\sqrt{2}}|1\rangle\right) \otimes \dots \otimes \left(\frac{1}{\sqrt{2}}|0\rangle + \frac{1}{\sqrt{2}}|1\rangle\right) \otimes |0\rangle \\ &= \left(\frac{1}{\sqrt{2}}\right)^n \sum_{x \in \{0,1\}^n} |x\rangle \otimes |0\rangle \quad (\text{!! "Unif. superpos. of all inputs"}) \end{aligned}$$

$$\therefore \text{output is } \left(\frac{1}{\sqrt{2}}\right)^n \sum_{x \in \{0,1\}^n} |x\rangle \otimes |F(x)\rangle$$

(all  $2^n$  answers encoded in state!!! But how to use....?)